1 功能说明

输入引脚: input(3bit), e1, ne2, ne3

输入引脚: output(8bit)

当 e1, ne2, ne3 为 100 时,38 译码器使能,正常工作。

仿真结果

Name	Value	0.000 ns		5.000 ns		10.000 ns			15.000 ns			
> ₩ input[2:0	7	0	1	2	3	4	5	6		7		
> ₩ outp:0]	ff	fe	fd	fb	f7	K	ff					
l⊌ e1	1											
₩ ne2	1											
¼ ne3	1											

主要代码

```
dibrary IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_arith.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;
entity decoder38_1 is
    port(
        e1 : in std_logic := '0';
        ne2 : in std_logic := '0';
        ne3 : in std_logic := '0';
        input: in std_logic_vector(2 downto 0);
        output: out std_logic_vector(7 downto 0));
end decoder38_1;
architecture Behavioral of decoder38_1 is
|begin
    output<= "111111110" when input="000" and el = '1' and ne2 = '0' and ne3 = '0'
        else "11111101" when input="001" and el = '1' and ne2 = '0' and ne3 = '0'
        else "11111011" when input="010" and el = '1' and ne2 = '0' and ne3 = '0'
        else "11110111" when input="011" and e1 = '1' and ne2 = '0' and ne3 = '0'
        else "11101111" when input="100" and el = '1' and ne2 = '0' and ne3 = '0'
        else "11011111" when input="101" and el = '1' and ne2 = '0' and ne3 = '0'
        else "10111111" when input="110" and e1 = '1' and ne2 = '0' and ne3 = '0'
        else "01111111" when input="111" and el = '1' and ne2 = '0' and ne3 = '0'
        else "111111111":
end Behavioral;
```